
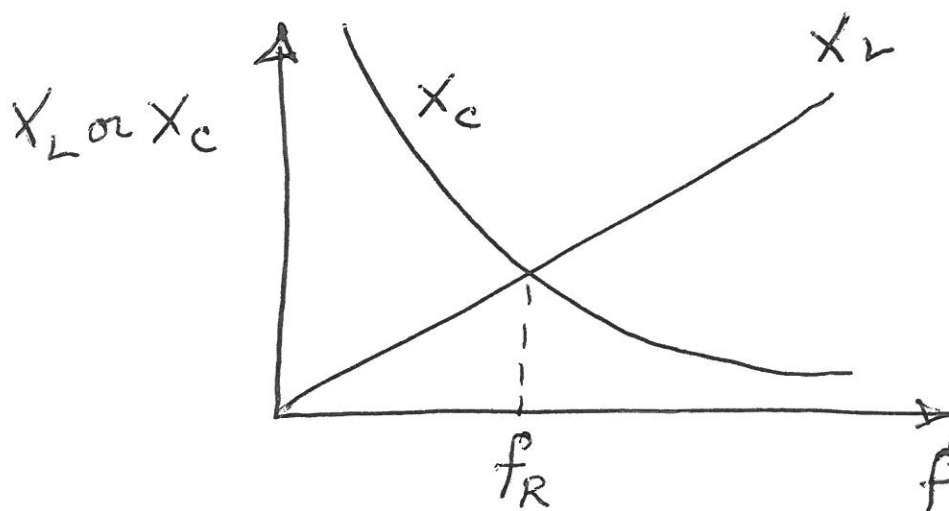
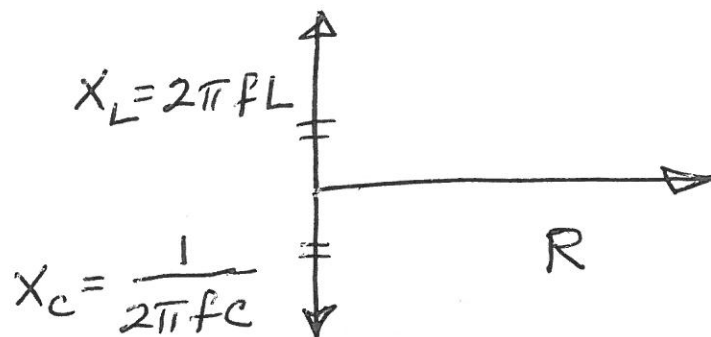


Physics 264 - Lecture 4

Resonant Circuit

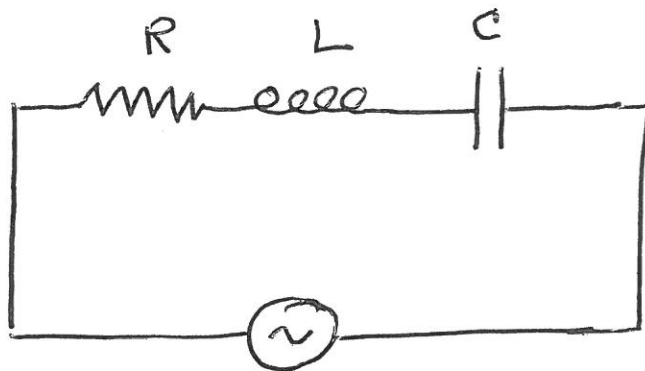

4-2

$$X_L = X_C$$

$$2\pi f_R L = \frac{1}{2\pi f_R C}$$

$$f_R = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$Z = \sqrt{\underbrace{(X_L - X_C)^2}_{=0} + R^2}$$

$Z = R$ at resonance


$$\theta = \tan^{-1} \left(\frac{\overbrace{X_L - X_C}^{=0}}{R} \right)$$

$$\boxed{\theta = 0^\circ}$$

4-3

Filters
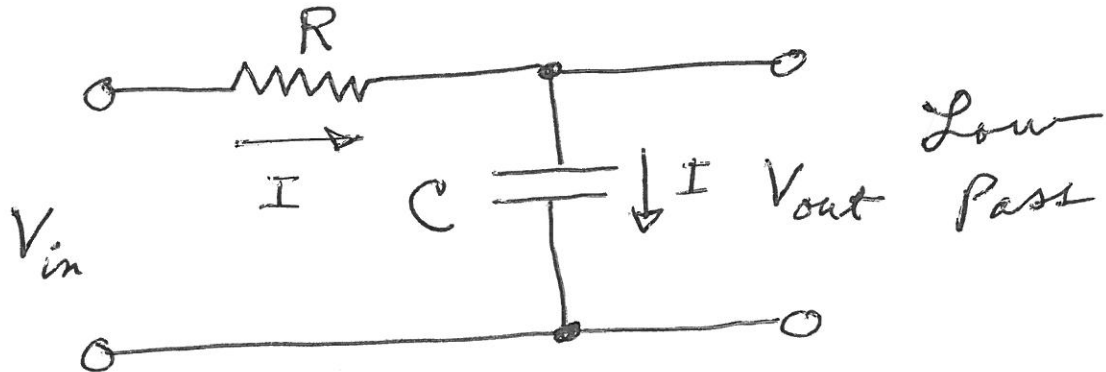
$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$





$$\frac{V_{out}}{V_{in}} = \frac{IX_c}{IZ} = \frac{X_c}{\sqrt{X_c^2 + R^2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{R}{X_c}\right)^2}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\omega \rightarrow 0 \quad \frac{V_{out}}{V_{in}} = 1$$

$$\omega \rightarrow \infty \quad \frac{V_{out}}{V_{in}} = 0$$

4-4

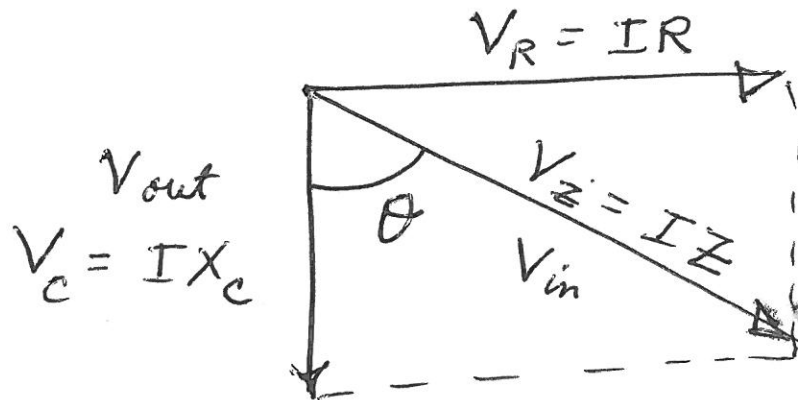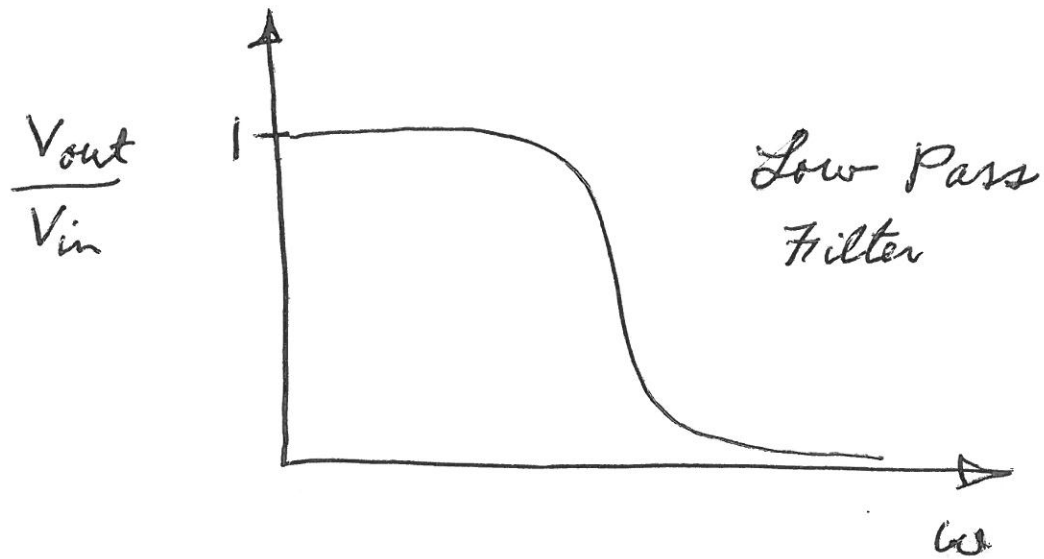


$$X_C = \frac{1}{2\pi fC}$$

$$\theta = \tan^{-1} \left(\frac{IR}{IX_C} \right)$$

$$\theta = \tan^{-1} (2\pi fRC)$$

4-5

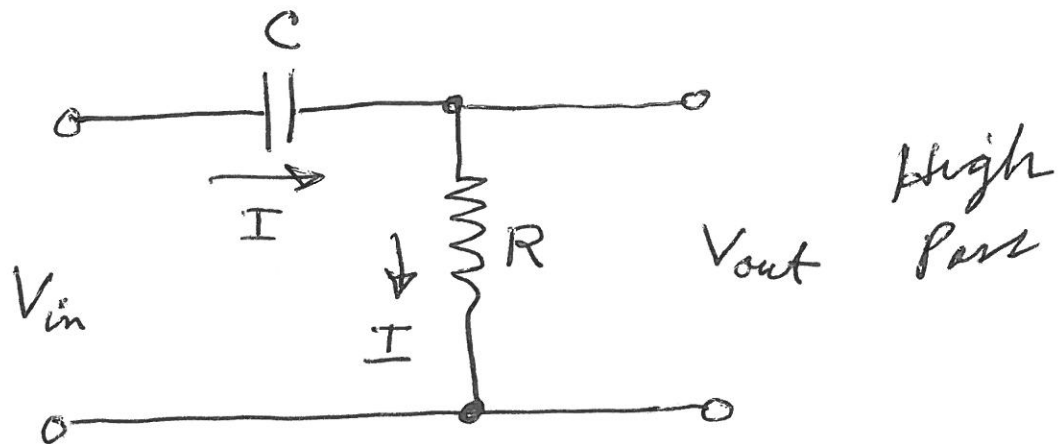

$$\frac{V_{out}}{V_{in}} = \frac{IR}{IZ} = \frac{R}{\sqrt{R^2 + X_c^2}}$$



$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{X_c}{R}\right)^2}} = \frac{1}{\sqrt{1 + \frac{1}{(2\pi fRC)^2}}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}}$$

$$\omega \rightarrow 0 \quad \frac{V_{out}}{V_{in}} = 0$$

$$\omega \rightarrow \infty \quad \frac{V_{out}}{V_{in}} = 1$$



4-6

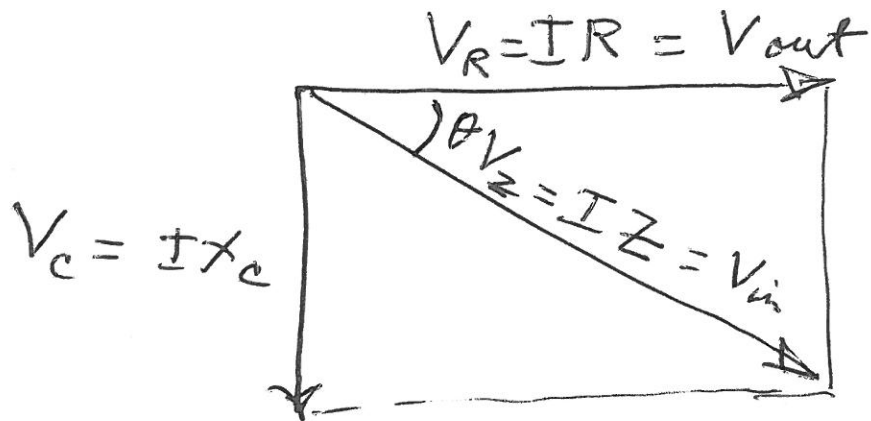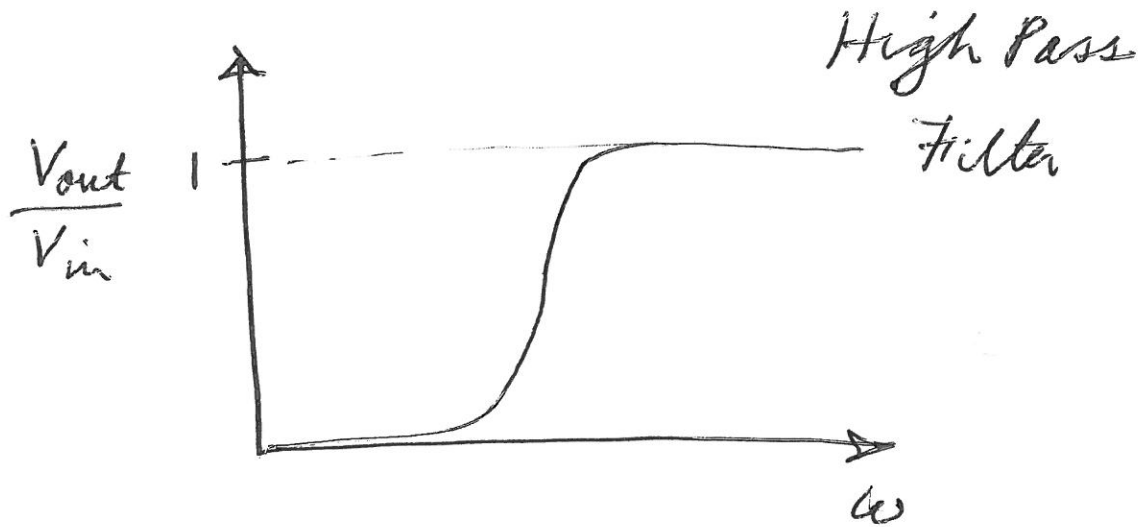

$$\theta = \tan^{-1} \left(\frac{IX_c}{IR} \right)$$


$$\theta = \tan^{-1} \left(\frac{1}{2\pi fRC} \right)$$

4-7

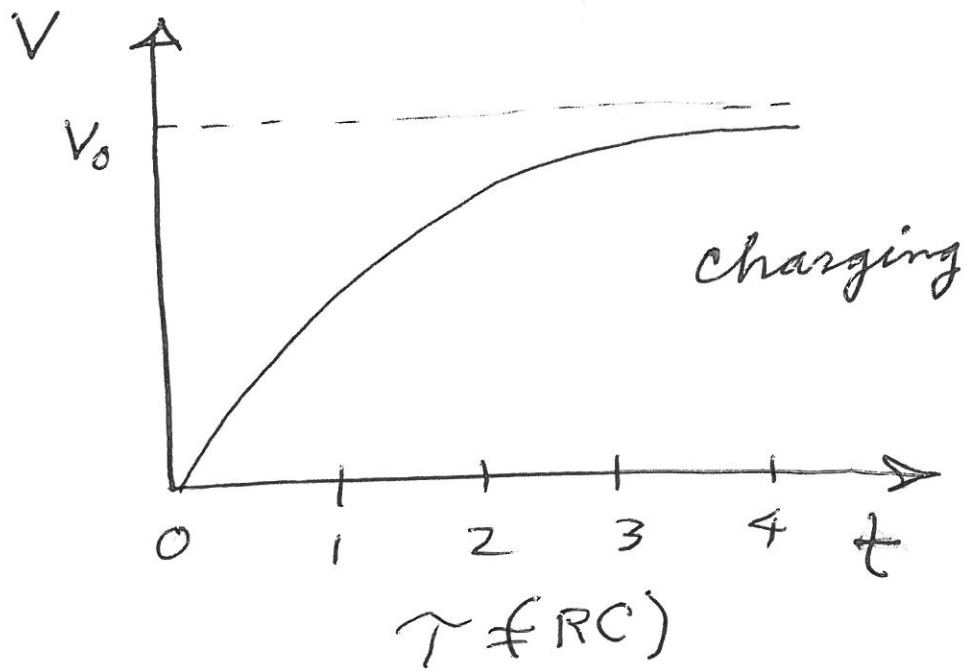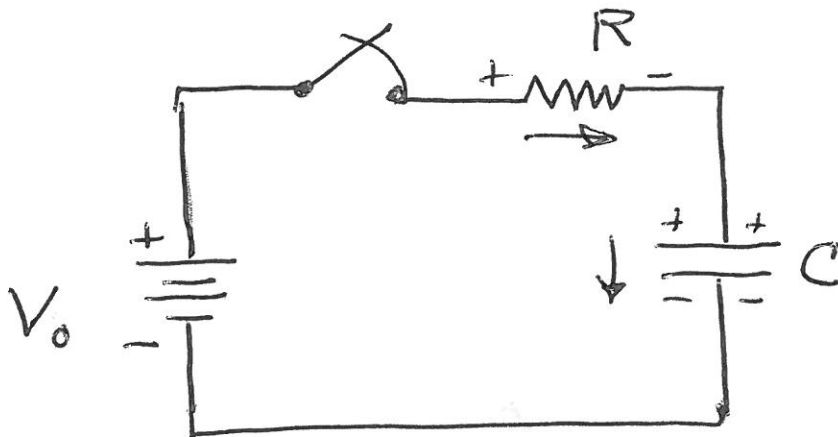

$$V = V_0 \left(1 - e^{-\frac{t}{RC}} \right)$$



4-8

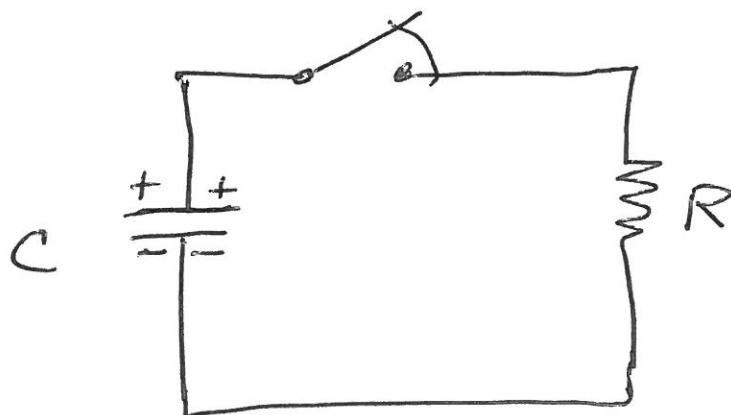

$$T = RC$$

$$V = V_0 e^{-\frac{t}{RC}}$$


4-9

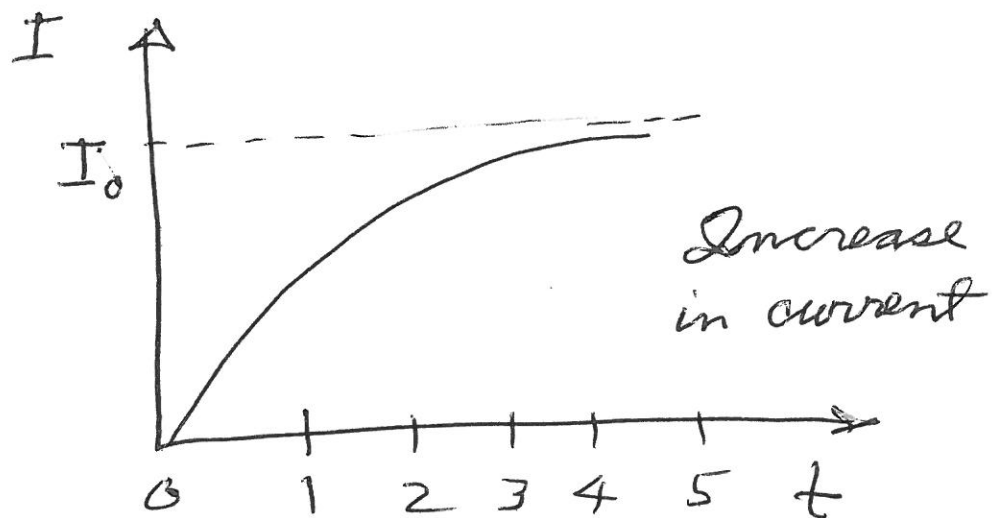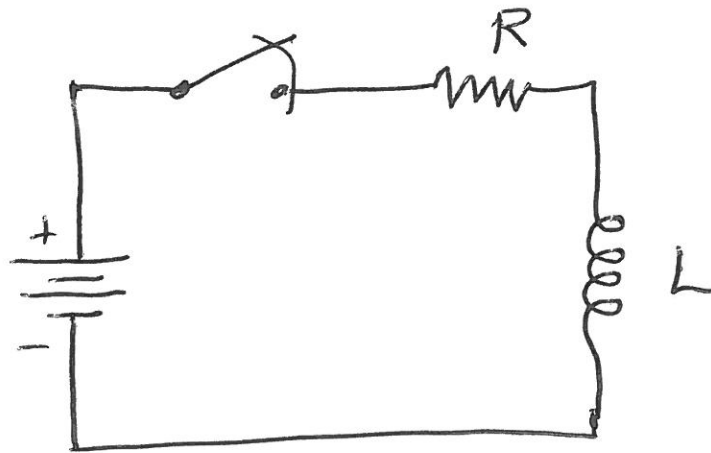

$$\tau = \frac{L}{R}$$

$$I = I_0 \left(1 - e^{-\frac{t}{\left(\frac{L}{R}\right)}} \right)$$


4-10

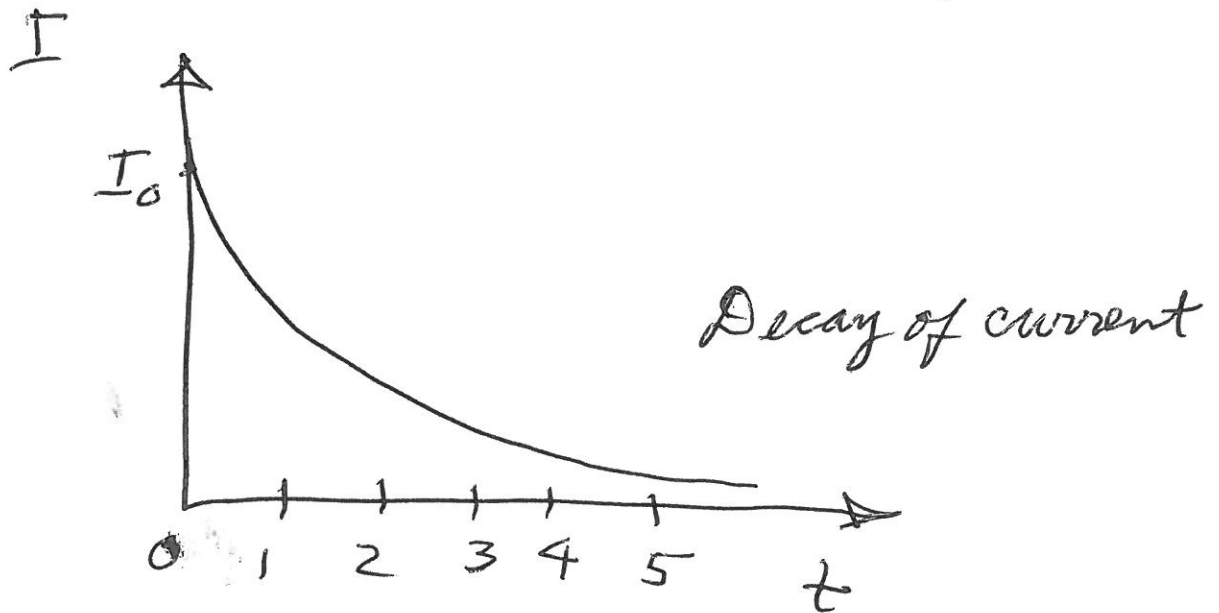

$$I = I_0 e^{-\frac{t}{\left(\frac{L}{R}\right)}}$$

4-11

Transformers

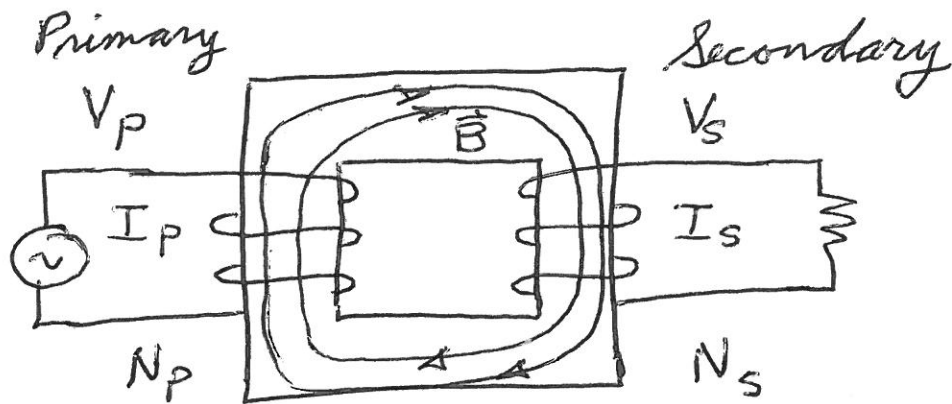

$$\frac{V_p}{V_s} = \frac{N_p \frac{d\Phi}{dt}}{N_s \frac{d\Phi}{dt}}$$

$\frac{d\Phi}{dt}$ = flux change

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{\text{number of turns Primary}}{\text{number of turns Secondary}}$$

$$\text{Power} = V_p I_p = V_s I_s$$

$$\frac{V_p}{V_s} = \frac{I_s}{I_p}$$