
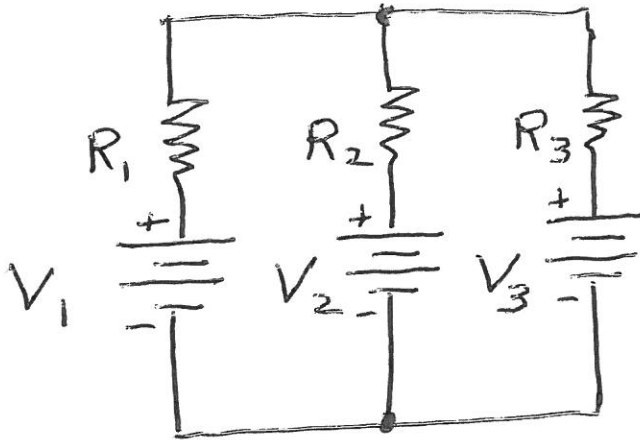


Physics 264 - Lecture 3

Millman's Theorem

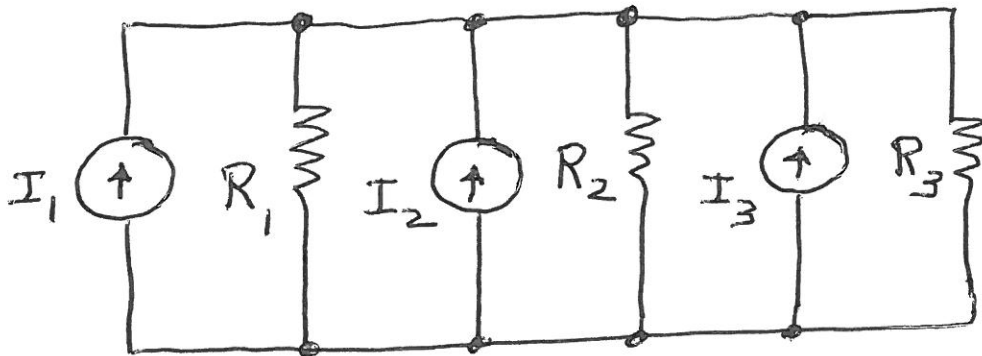


Transform to Norton's Circuit



$$I_1 = \frac{V_1}{R_1} \quad I_2 = \frac{V_2}{R_2} \quad I_3 = \frac{V_3}{R_3}$$
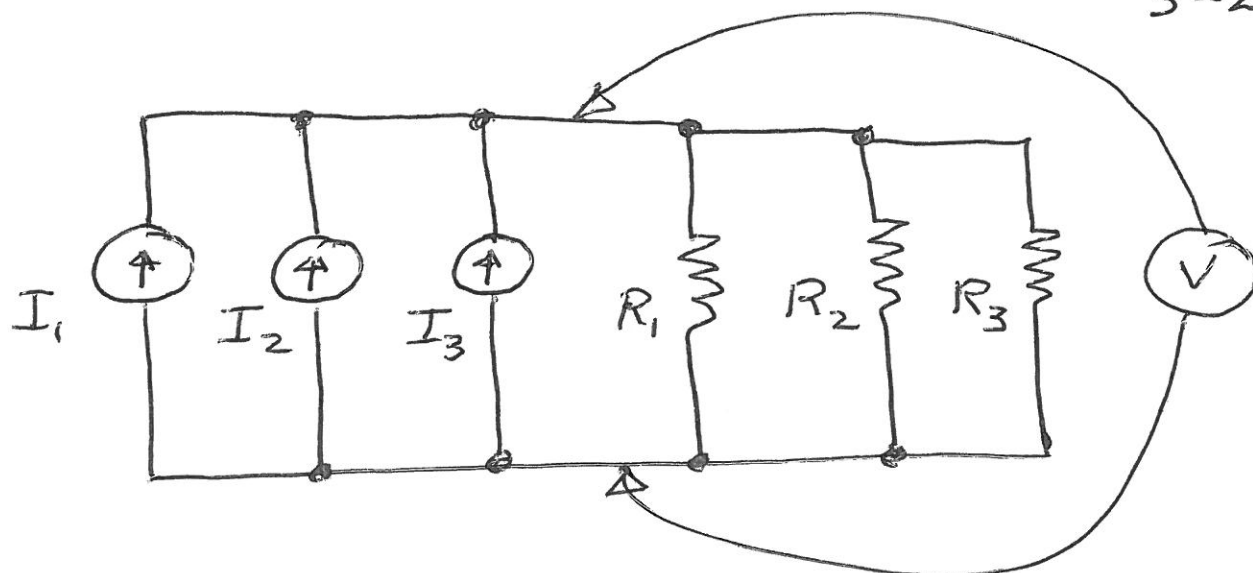
$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$




$$V = (I_1 + I_2 + I_3) R$$



$$V = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

AC Circuit

$$V = IR$$

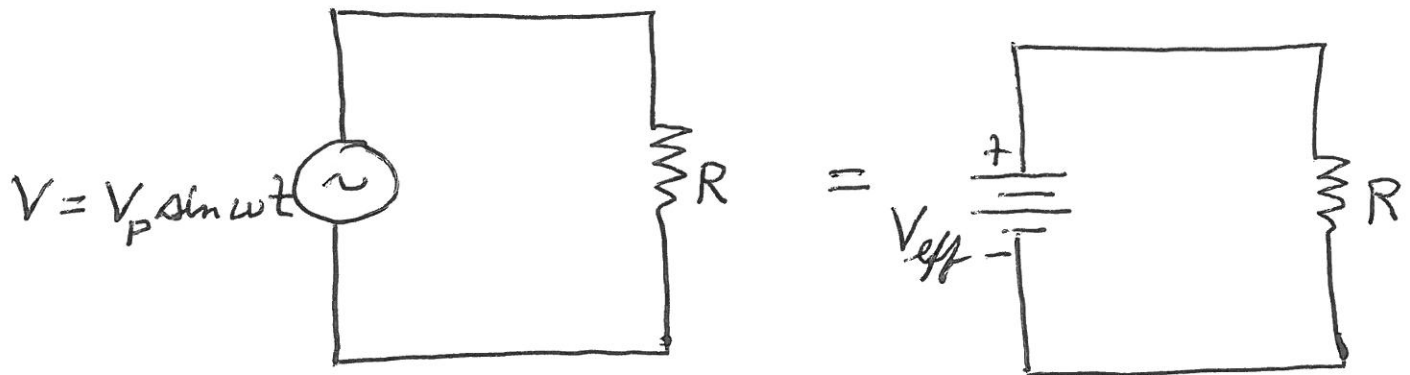

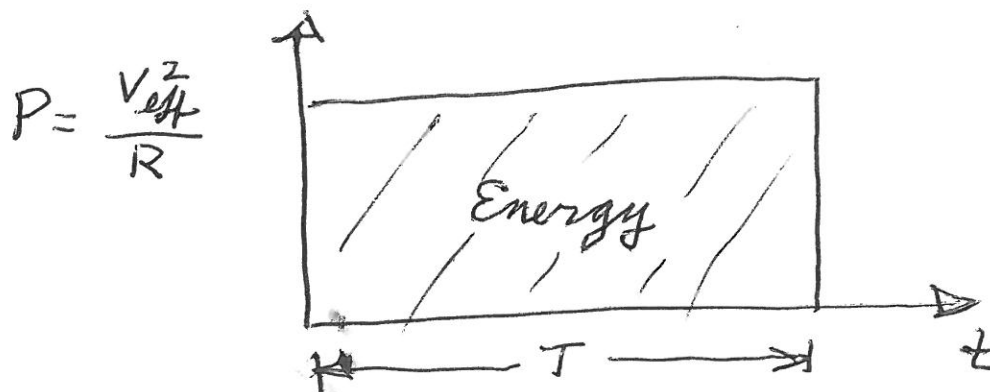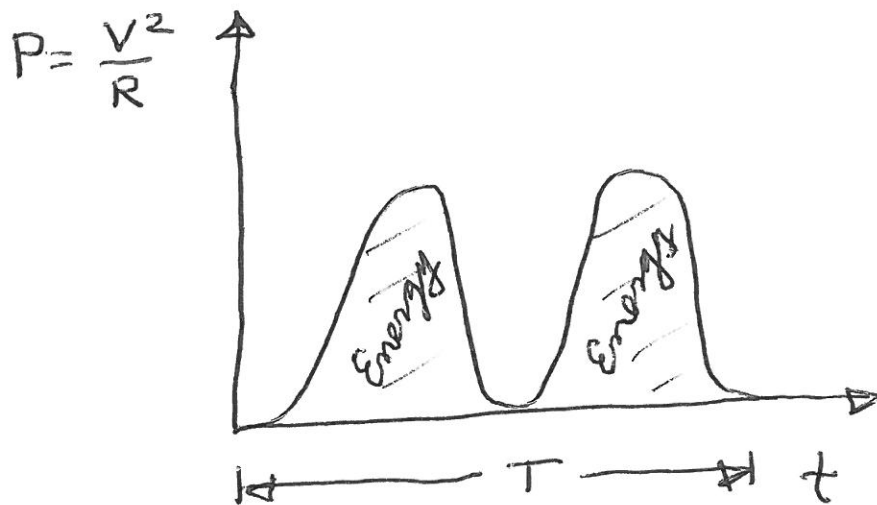
$$P = \text{Power} = IV = I^2 R = \frac{V^2}{R}$$



$$\text{Energy} = \int_0^T \frac{V^2}{R} dt = \frac{V_{\text{eff}}^2}{R} T$$

$$\text{Energy} = \frac{\overline{V^2}}{R} T = \frac{V_{\text{eff}}^2}{R} T$$


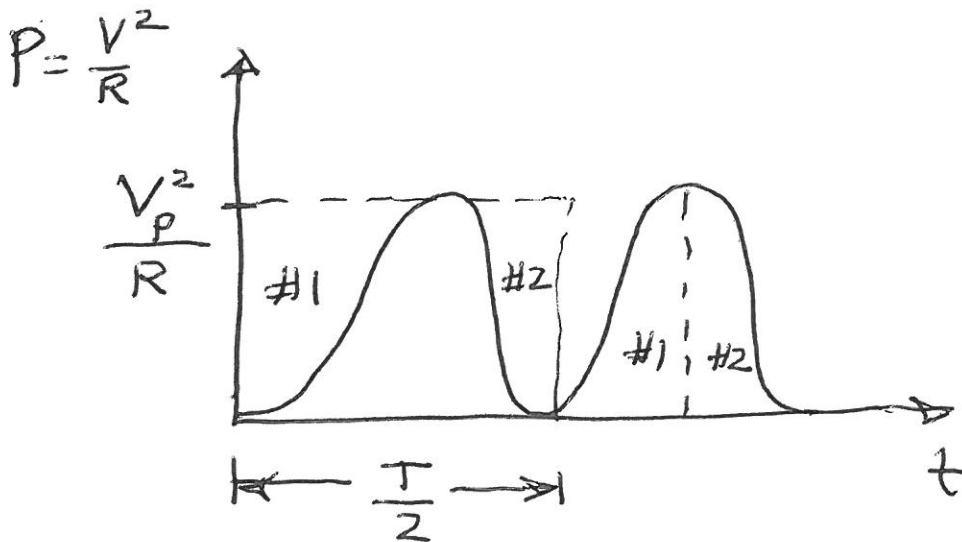
$$V_{\text{eff}} = \sqrt{\overline{V^2}} \begin{matrix} \leftarrow \text{root} \\ \nearrow \text{mean} \\ \nwarrow \text{square} \end{matrix} = V_{\text{rms}}$$



$$\frac{V_P^2}{R} \frac{T}{2} = \frac{V_{\text{rms}}^2}{R} T$$

$$V_{\text{rms}} = \frac{V_P}{\sqrt{2}} \quad \text{Sine Wave}$$



Triangle Wave

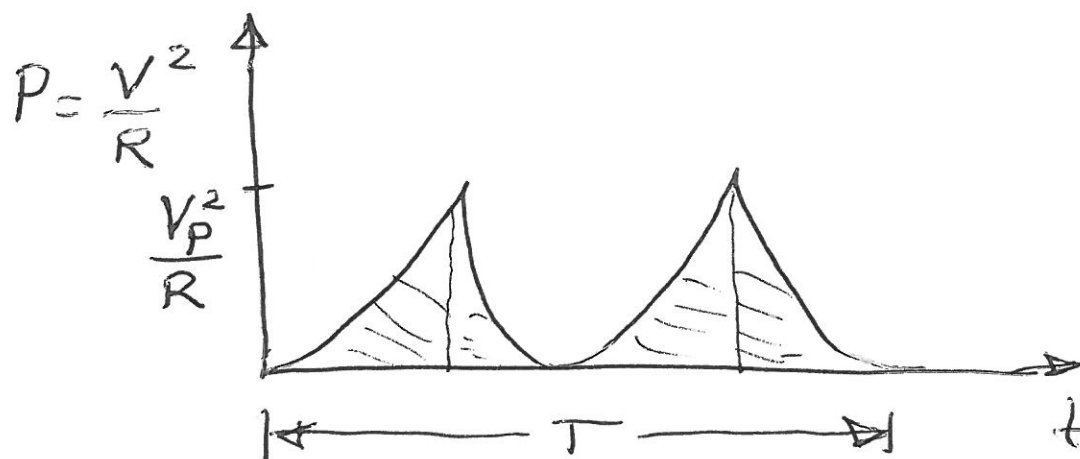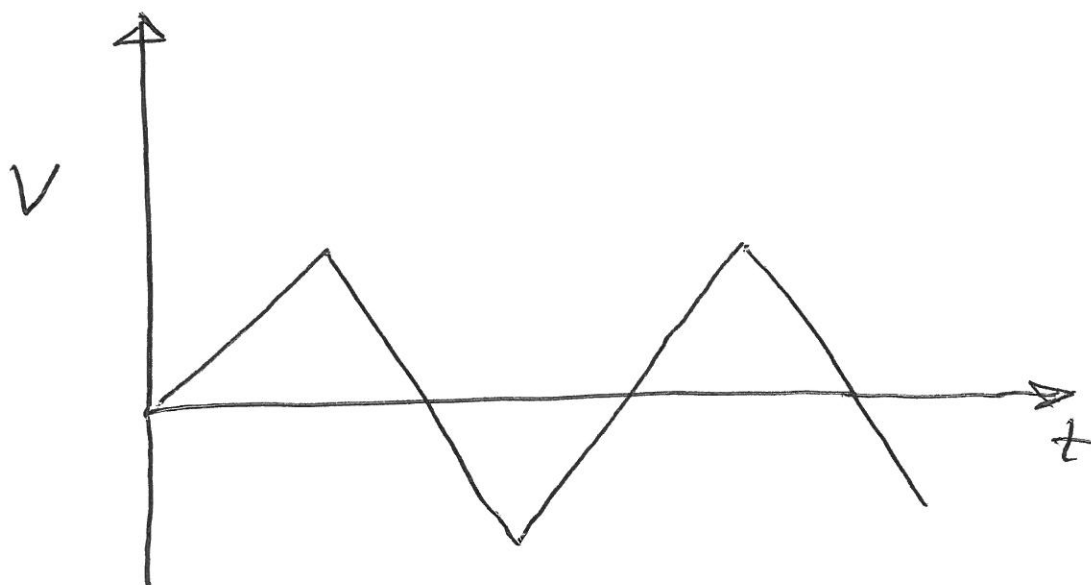

$$\left(\frac{1}{3}\right) \left(\frac{T}{T}\right) \frac{V_P^2}{R} = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_P}{\sqrt{3}} \quad \text{Triangle Wave}$$


3-6

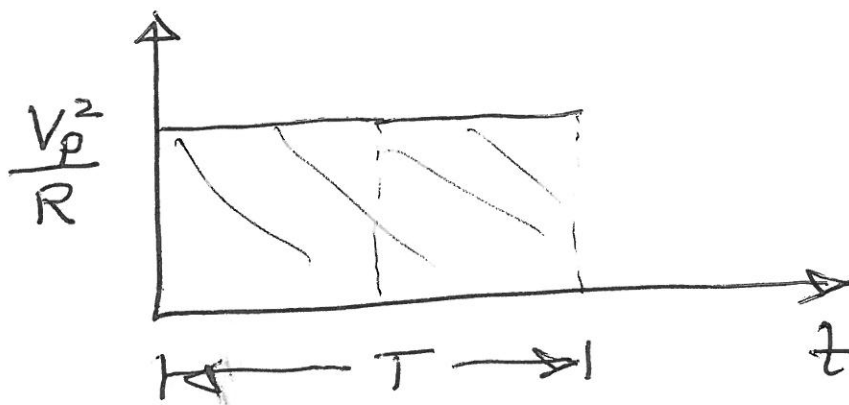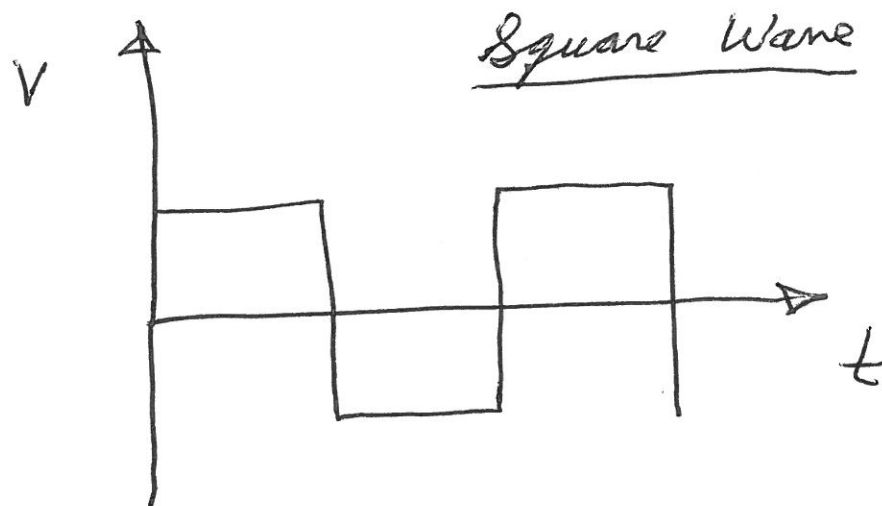

$$\frac{V_p^2}{R} T = \frac{V_{rms}^2}{R} T$$


$$V_{rms} = V_p \quad \text{Square Wave}$$

Resistor

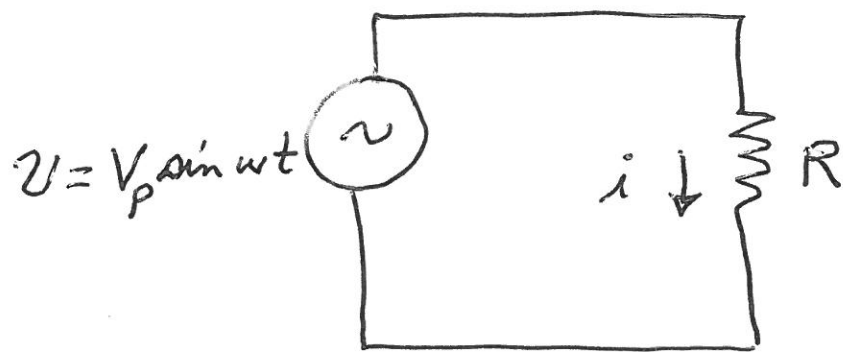


$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R}$$
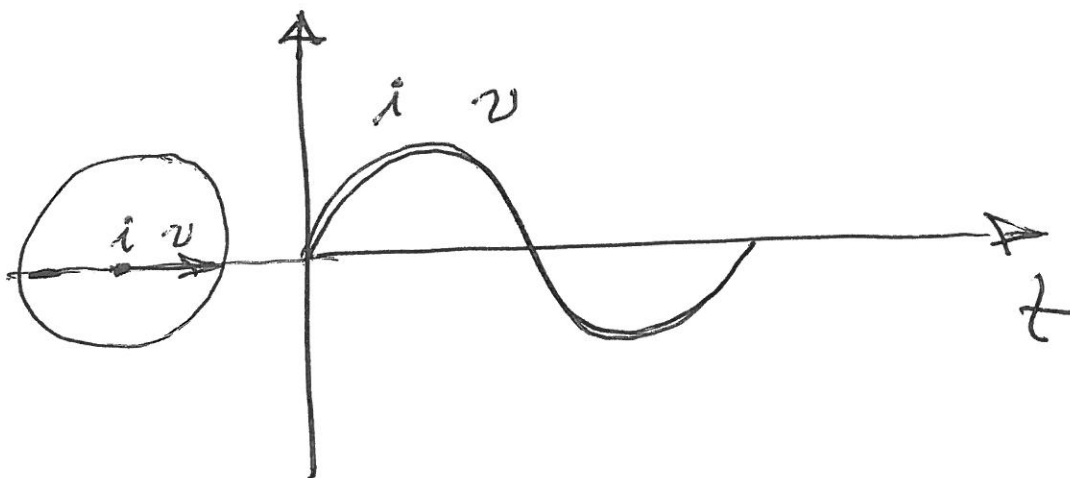
$$I = \frac{V}{R} \quad \text{rms values}$$



i and v are in phase

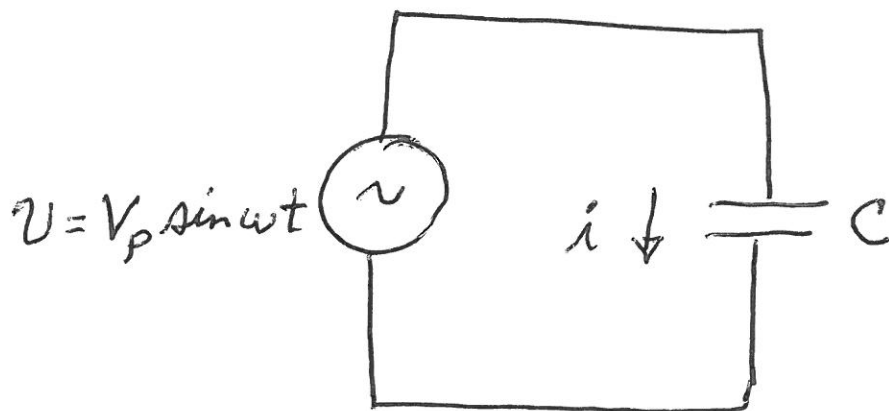

$$q = C v$$

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C V_p \omega \cos \omega t$$


$$i = \frac{V_p \cos \omega t}{\left(\frac{1}{\omega C}\right)}$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$


$$I = \frac{V}{X_c} \quad \text{rms values}$$

$$X_c = \frac{1}{\omega C} \quad \text{units of ohm}$$

3-9

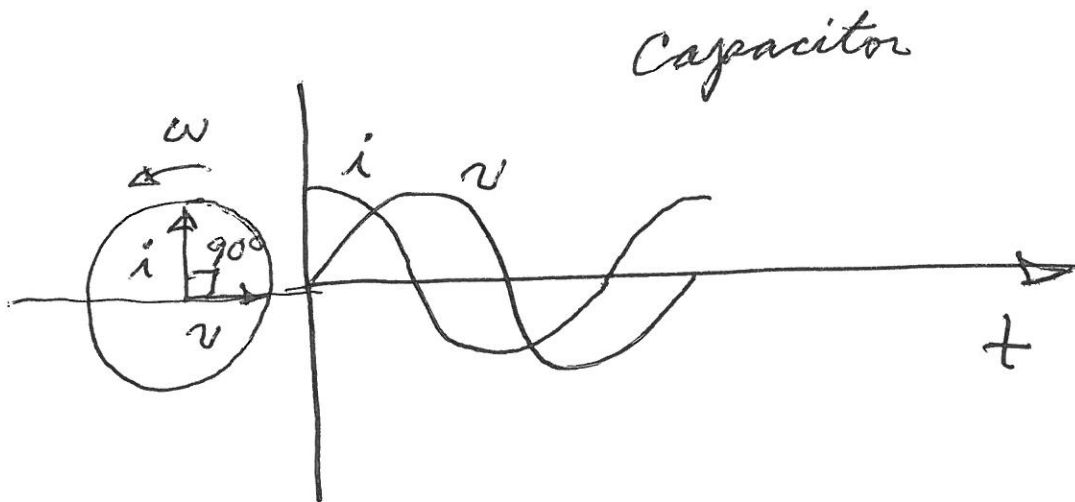

current i leads voltage v by 90°

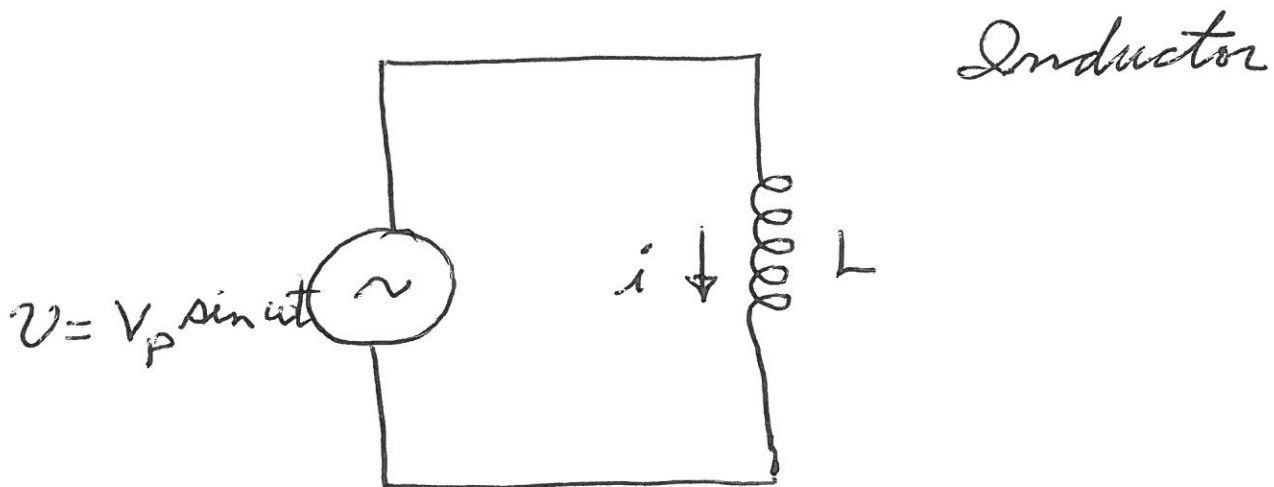

$$v = L \frac{di}{dt}$$

$$i = \int di = \frac{1}{L} \int v dt$$

$$i = \frac{1}{L} \int V_p \sin \omega t dt$$


$$i = - \frac{V_p \cos \omega t}{\omega L}$$

$$I = \frac{V}{\omega L}$$



$$X_L = \omega L = 2\pi f L$$

$$I = \frac{V}{X_L}$$

X_L units of ohm

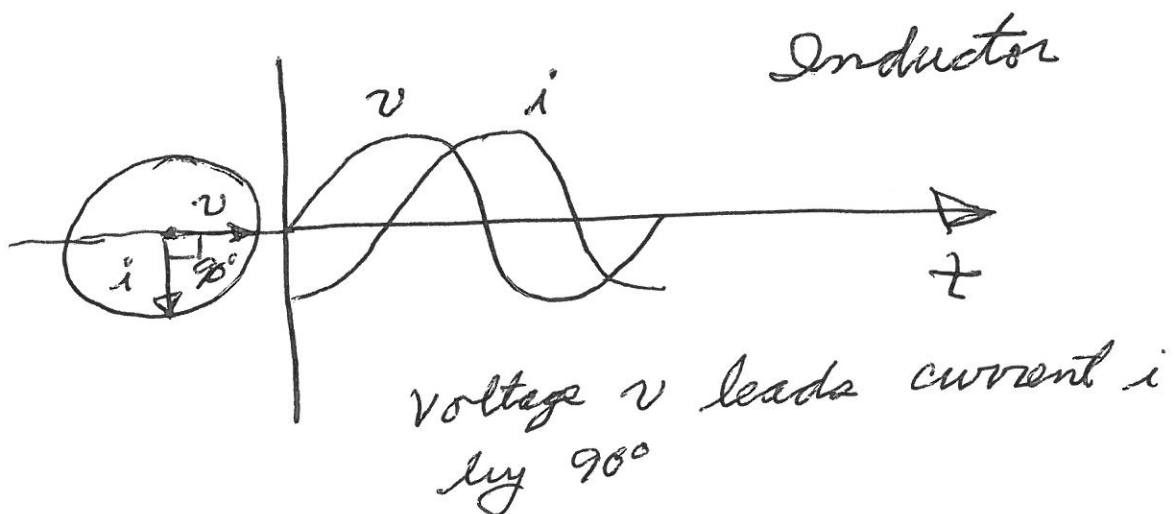


3-11

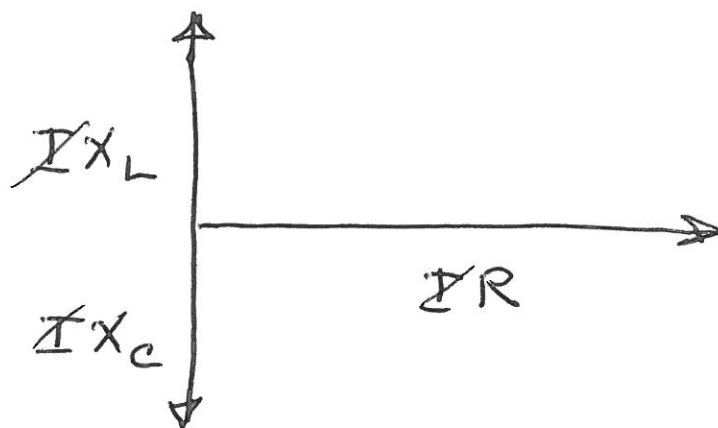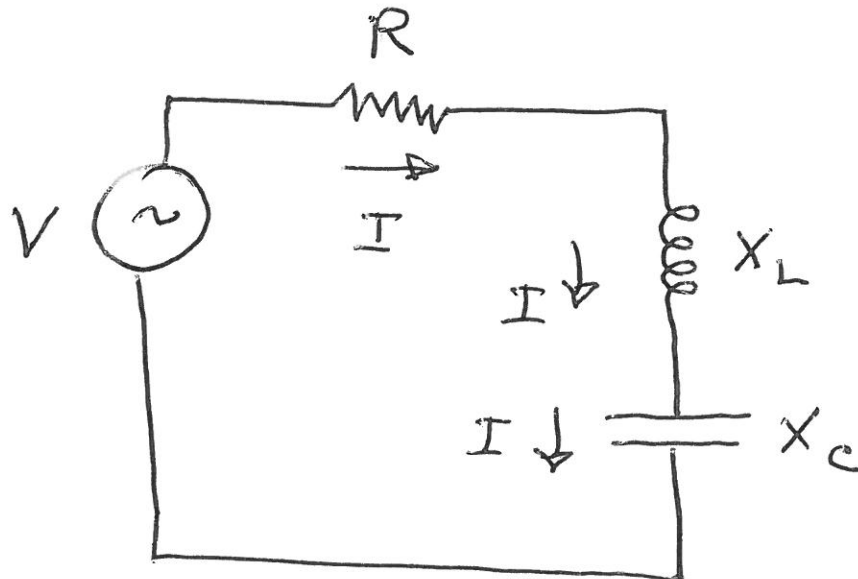

Impedance



Diagram

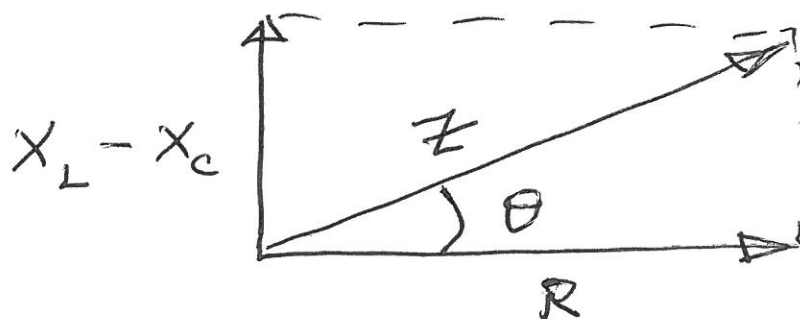

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

3-12
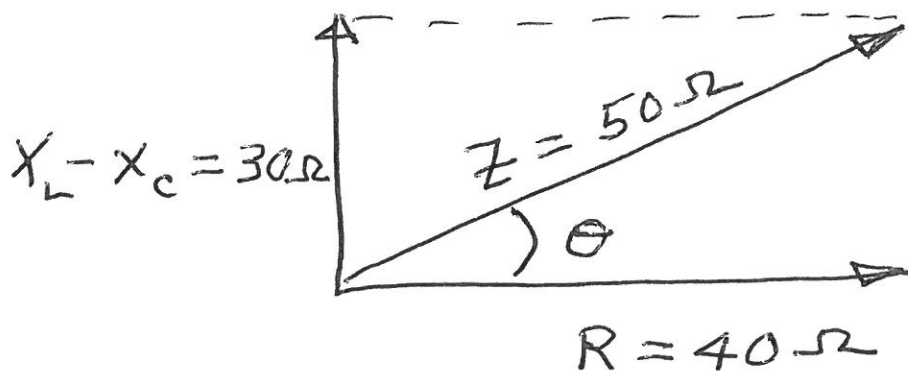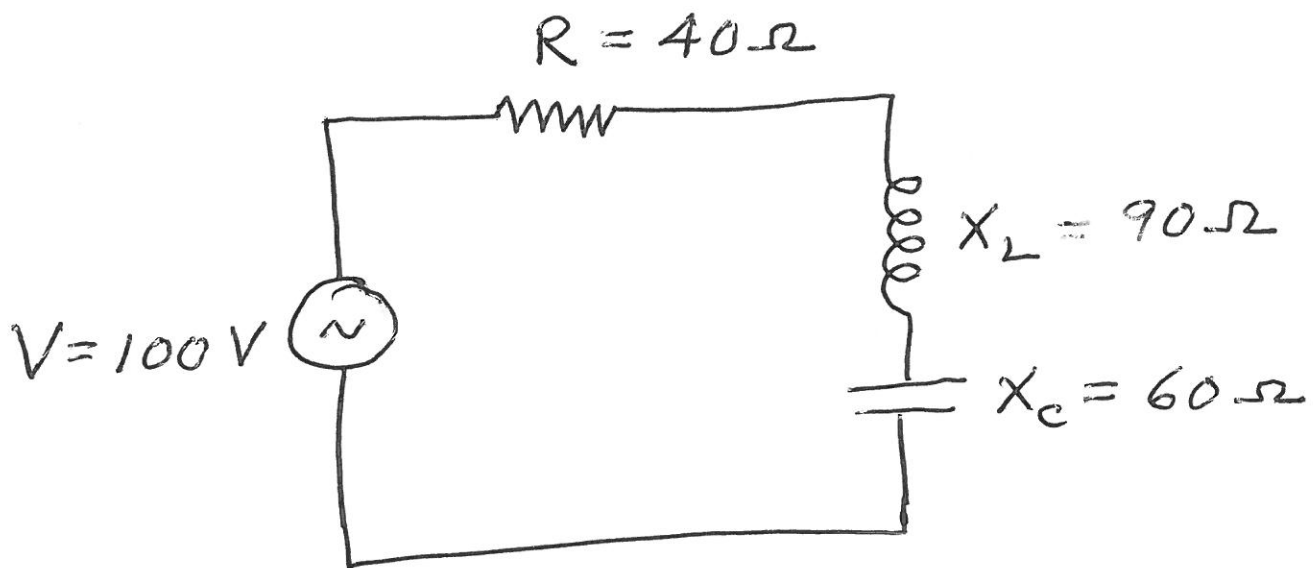
$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$



$$Z = \sqrt{30^2 + 40^2} = \sqrt{2500} = 50\ \Omega$$

$$I = \frac{100}{50} = 2\text{ A} \quad \theta = \tan^{-1} \left(\frac{30}{40} \right) = 37^\circ$$