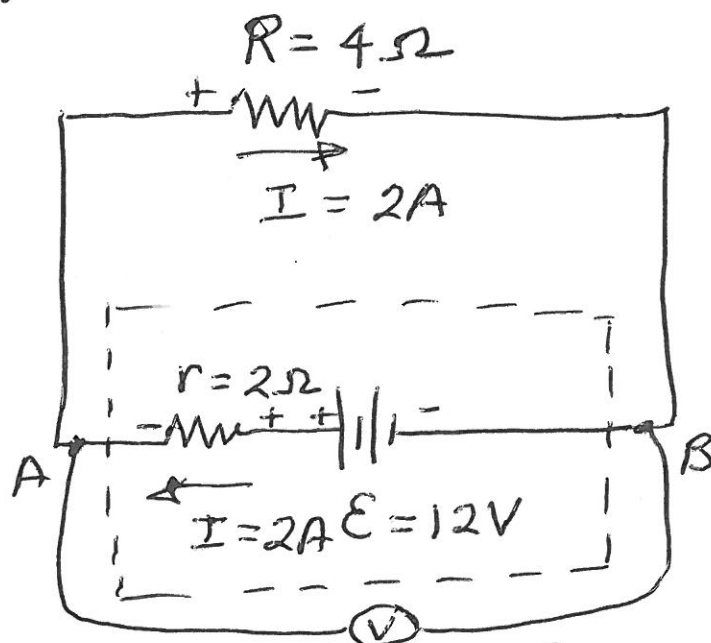


Physics 264 - Lecture 1

Effect = constant \times cause

$$I = GV = \left(\frac{1}{R}\right)V$$

\uparrow current (A) \uparrow conductance \nwarrow potential difference (V) \nearrow resistance (Ω)



Battery with $\text{emf} = 12V$ and internal resistance of $r = 2\Omega$

$$I = \frac{\mathcal{E}}{R + r} = \frac{12}{4 + 2} = \frac{12}{6} = 2A$$


$$V_{AB} = \mathcal{E} - Ir = 12 - (2)(2) = 8V$$

Microscopic View

Effect = constant \times cause

$$\vec{J} = \sigma \vec{E} = \frac{1}{\rho} \vec{E}$$

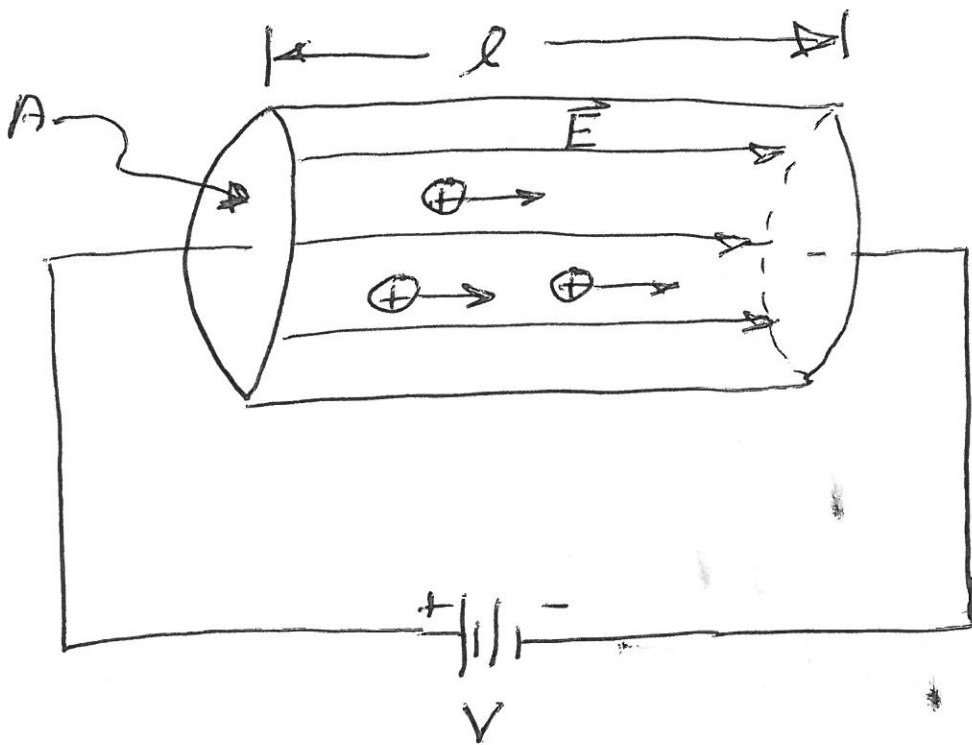\vec{J} \rightarrow current density
 σ \rightarrow conductivity
 ρ \rightarrow resistivity
 \vec{E} \rightarrow electric field



$$I = \int \vec{J} \cdot d\vec{a} \quad \vec{E} = -\vec{\nabla} V$$


$$J = \frac{1}{\rho} E$$

$$\frac{I}{A} = \frac{1}{\rho} \left(\frac{V}{\ell} \right)$$


$$\frac{V}{I} = \rho \frac{\ell}{A}$$


$$R = \rho \frac{\ell}{A}$$

Linear
graphs

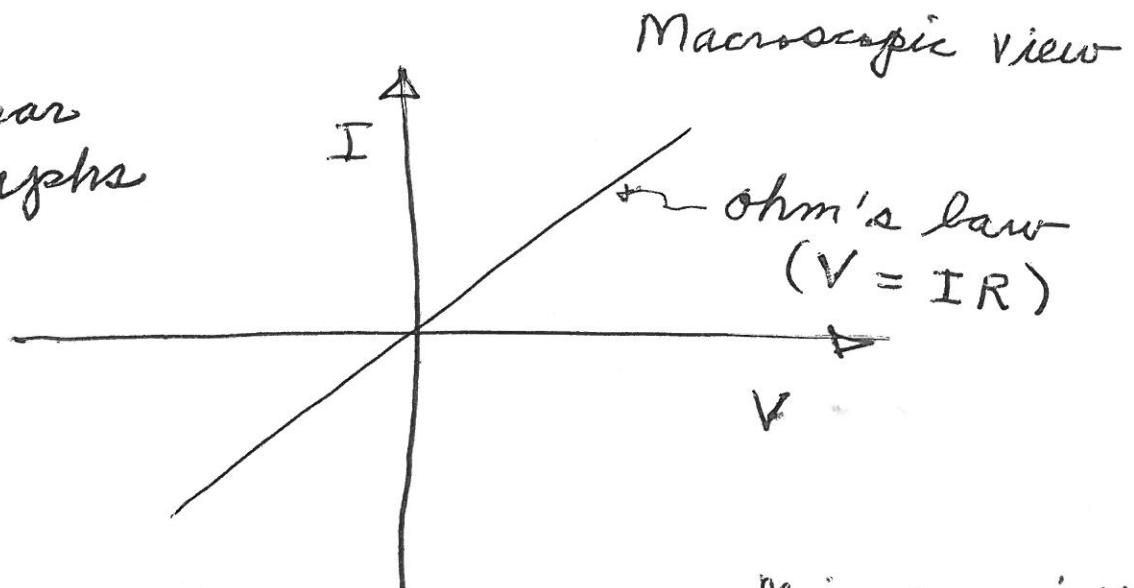

Microscopic view

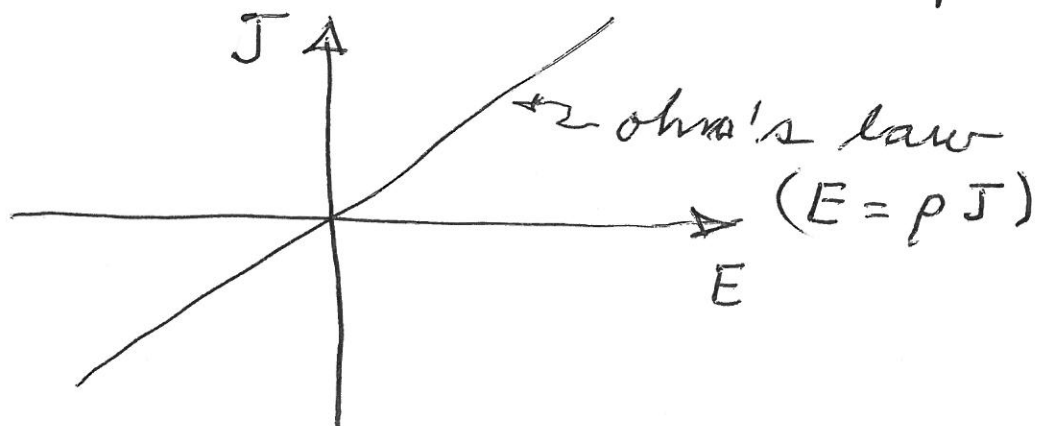

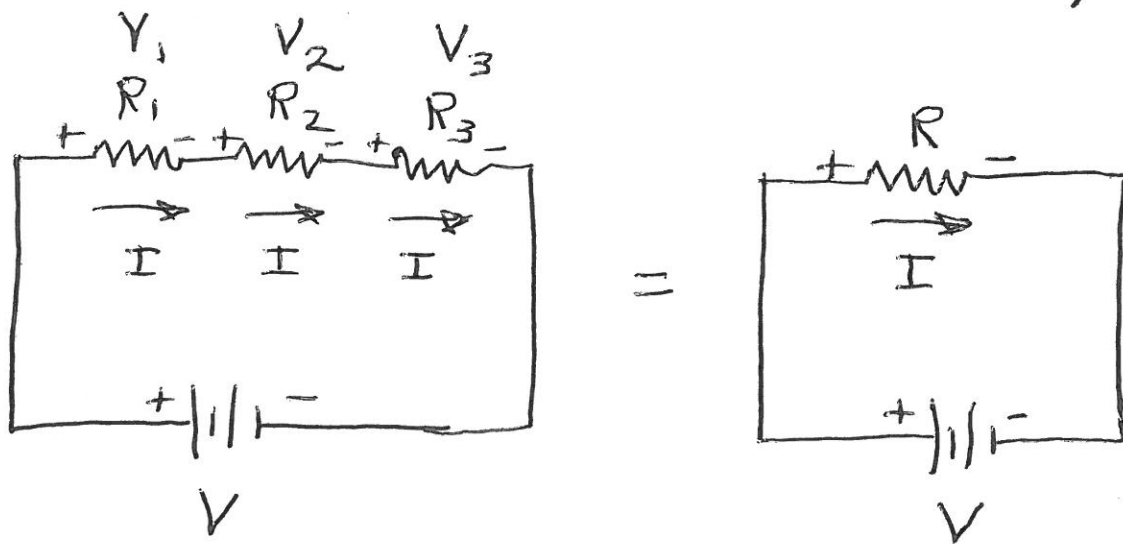


series resistors

$$V = V_1 + V_2 + V_3$$

$$IR = IR_1 + IR_2 + IR_3$$

$$\boxed{R = R_1 + R_2 + R_3}$$

1-5

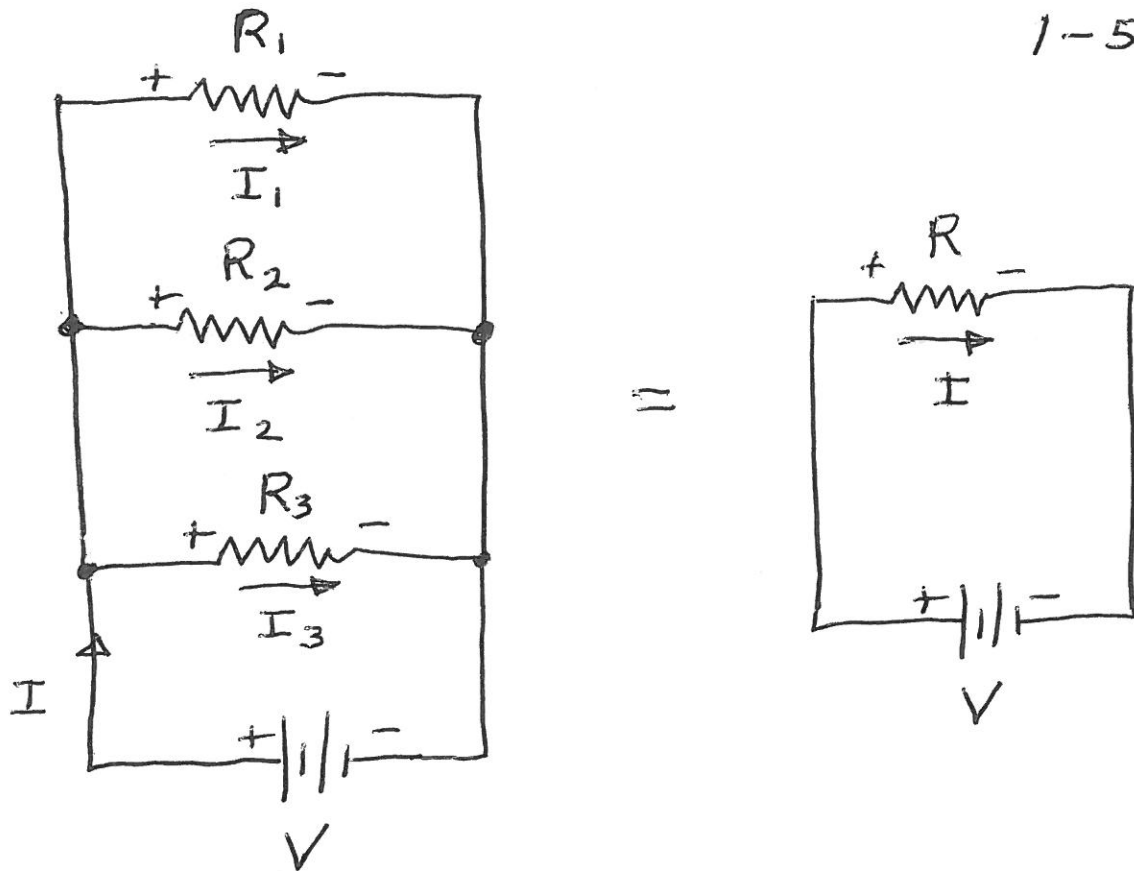


Parallel resistors

$$I = I_1 + I_2 + I_3$$


$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

1-6

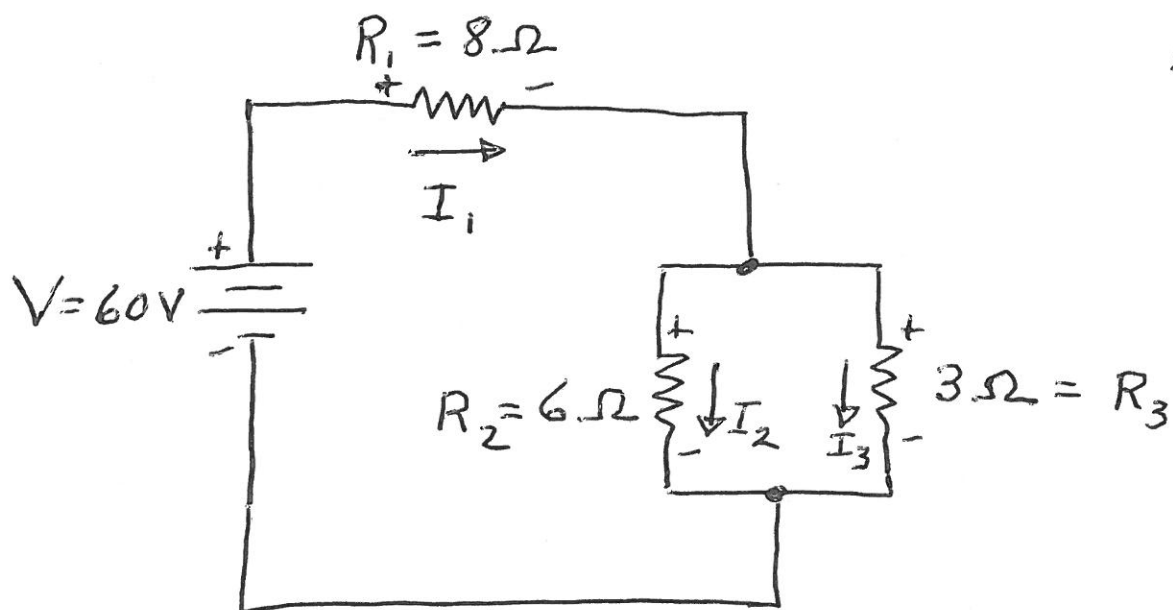
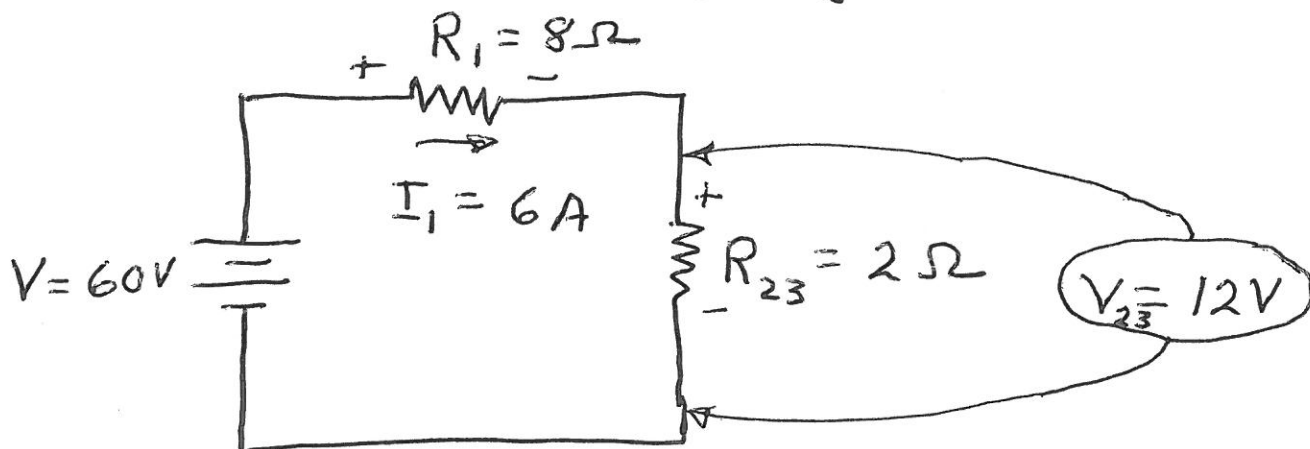
$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = \frac{(6)(3)}{6 + 3} = 2\Omega$$



$$V_{23} = 60 - 48 = 12V$$

